
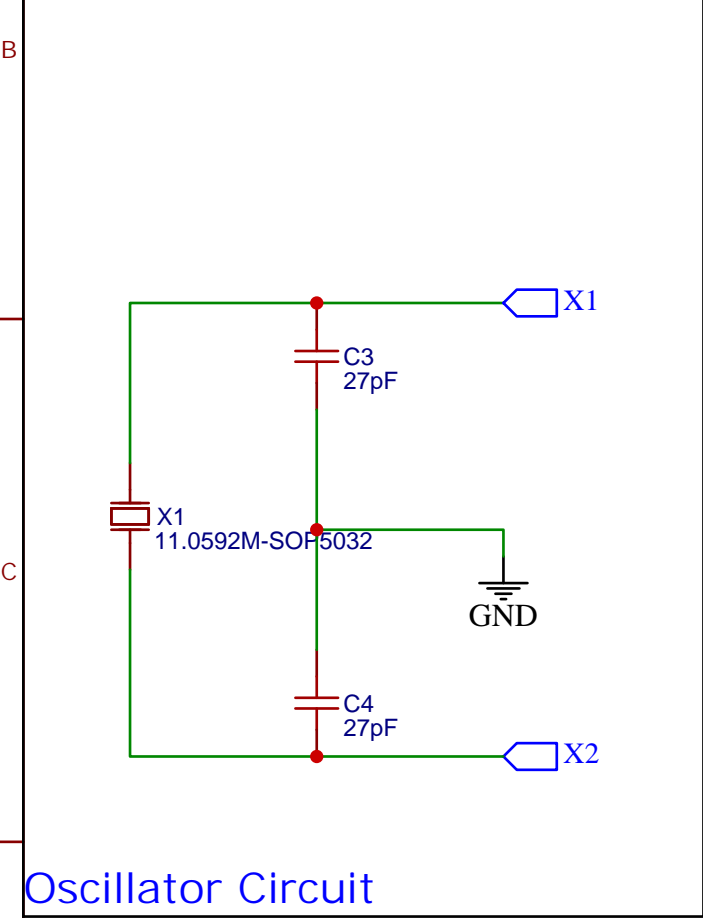


Power Supply Circuit



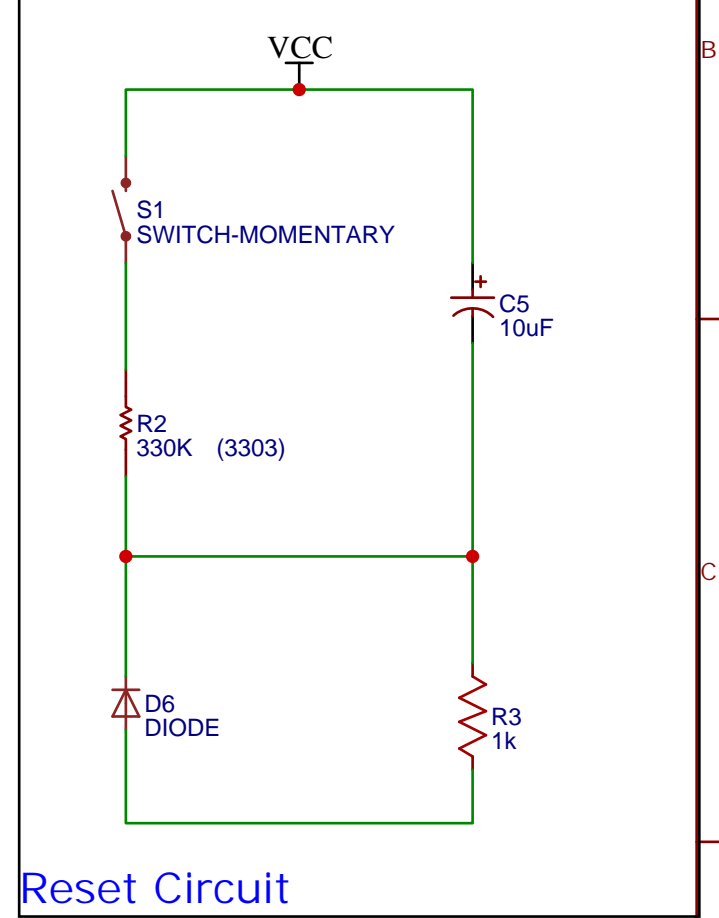


Oscillator Circuit



Reset Circuit



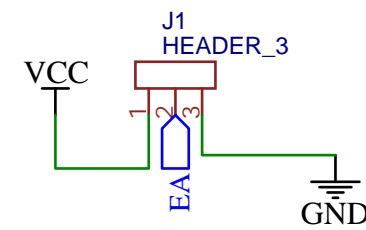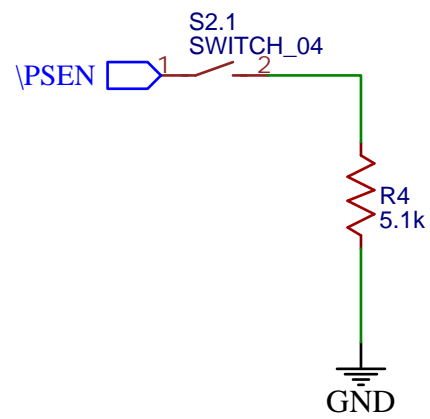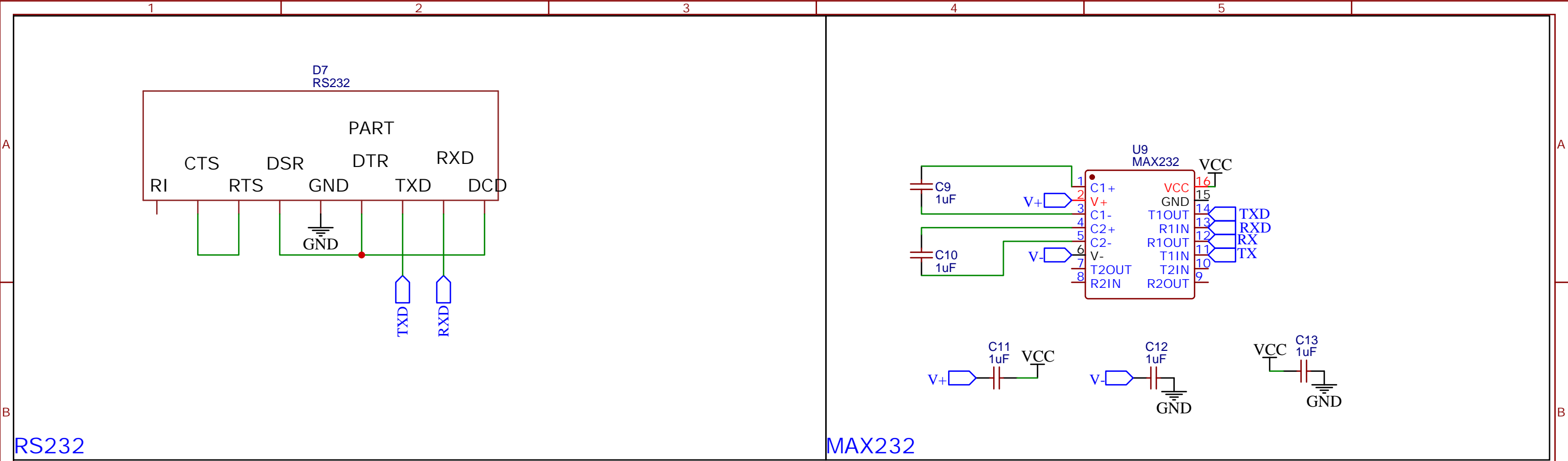

TITLE: Lab 2		REV: 1.0
	Company: University of Colorado Boulder	Sheet: 1/3
	Date: 2022-02-18	Drawn By: Abijith A