
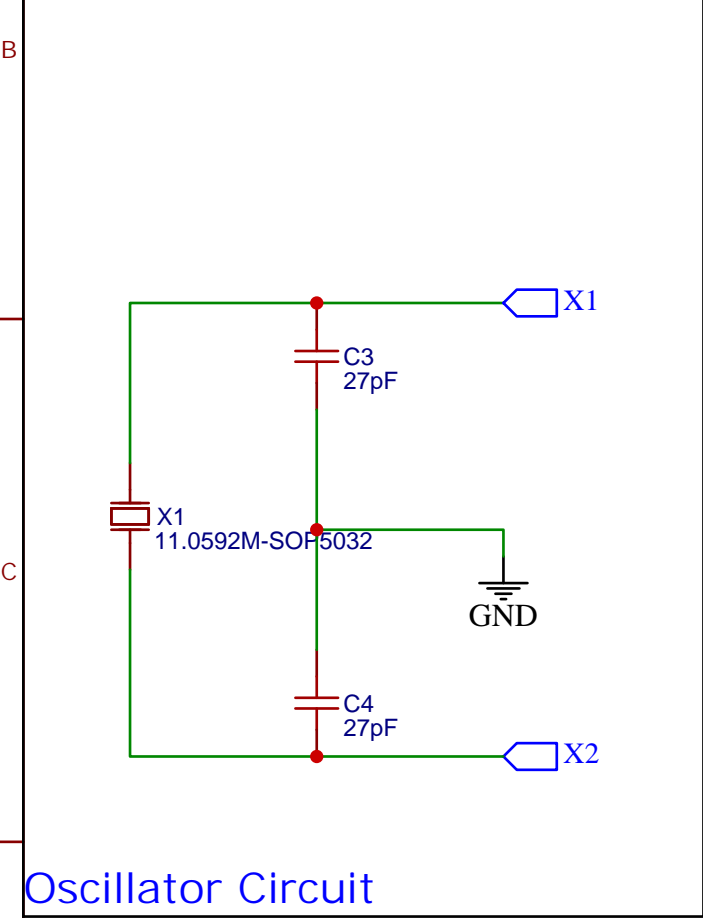





Power Supply Circuit

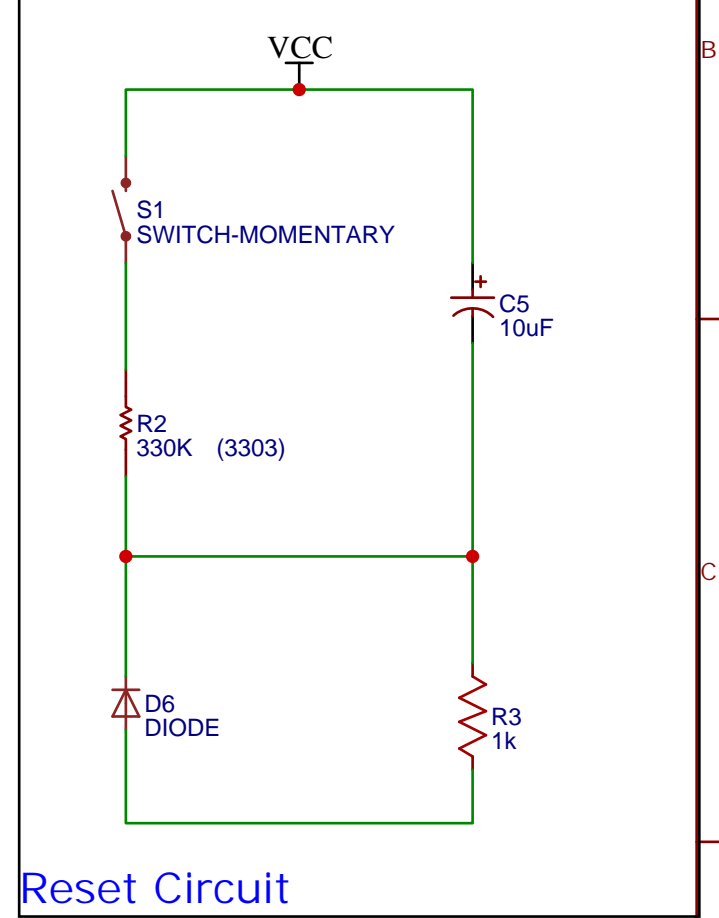

Oscillator Circuit






Reset Circuit

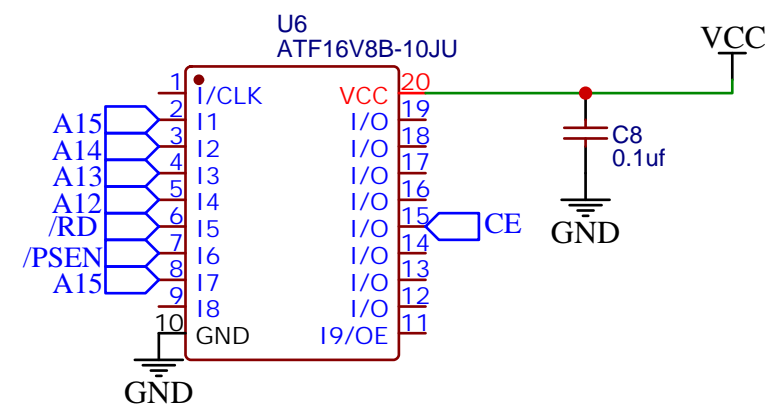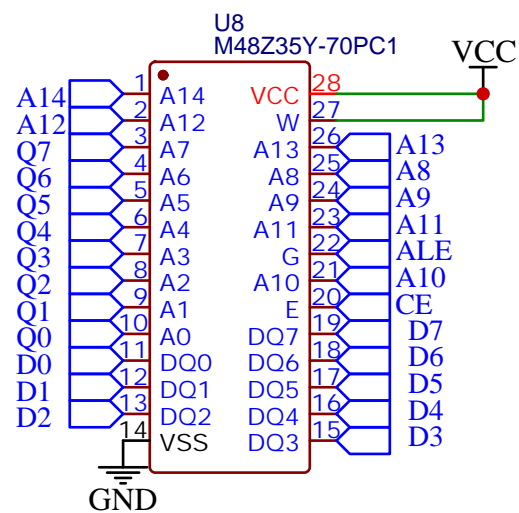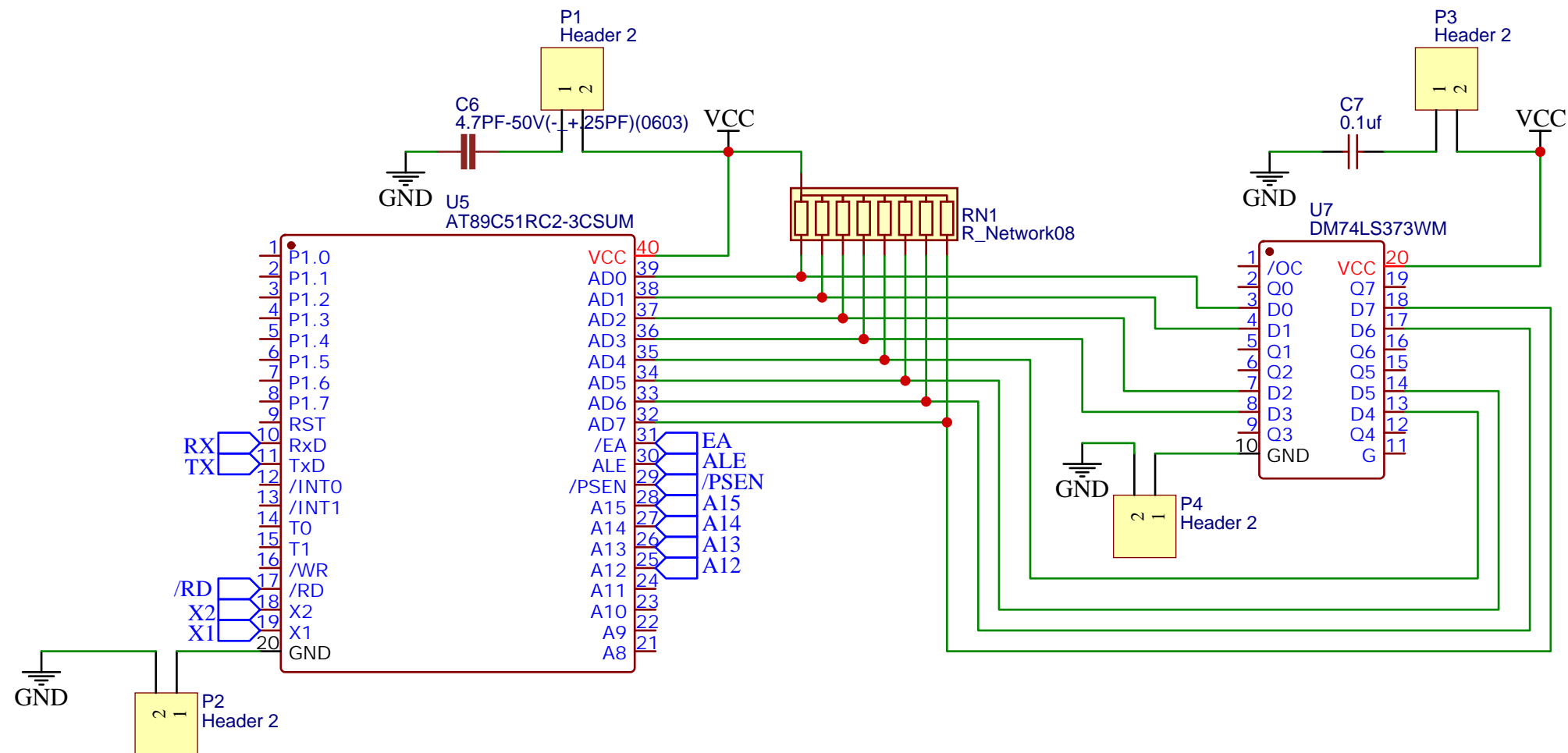

Microchip (Atmel) ATF16V8C SPLD, DIP-20

TITLE: Lab1_Part3_Schematic_2		REV: 1.0
EasyEDA	Company: University of Colorado Boulder	Sheet: 2/2
	Date: 2022-02-06	Drawn By: Abijith A

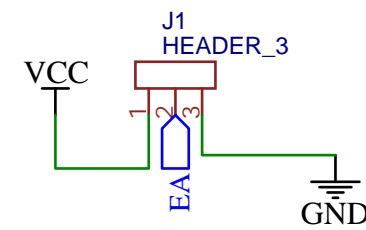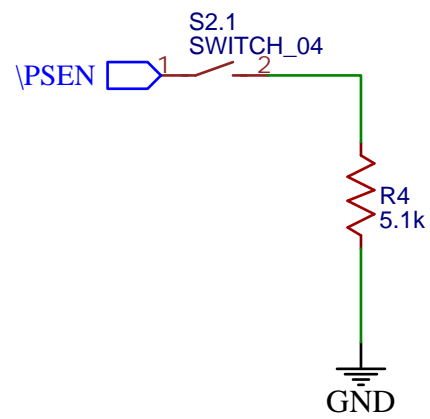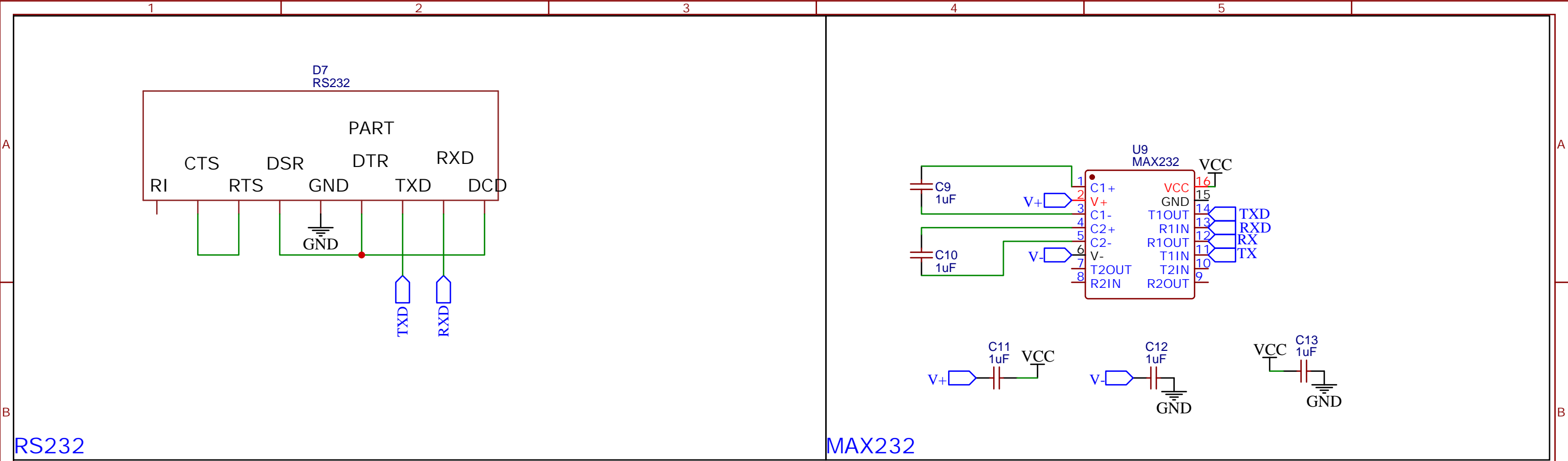

TITLE: Lab 2		REV: 1.0
EasyEDA	Company: University of Colorado Boulder	Sheet: 1/3
	Date: 2022-02-18	Drawn By: Abijith A